When a Capacitor is Connected to adc Source The Voltage rises from 20V to 36V in 4 Ms with an average charging current of 0.6A. Determine the value of the Capacitance. Calculat the change in the energy Stord in the Capacitor During this period of time!

Q = C.V = I.t $Q = C.\Delta V = I.\Delta t$ $C(36-20) = 0.6 + 4 + 10^{-6}$


$$C = \frac{0.6 \times 4 \times 10^{-6}}{16} = 1.5 \times 10^{7} = 0.15$$

 $W = \frac{1}{2}CV^{2}$ $= \frac{1}{2}CV^{2} - \frac{1}{2}CV^{2}$ $= \frac{1}{2}(0.15 * 10^{6})[(36)^{2}(20)^{3}]$

and two possible trees. what is the number of necessary node and Loop equations? Find the power disripated in the resistance R when the Carrent in the branch AO:

Solution.

Graph

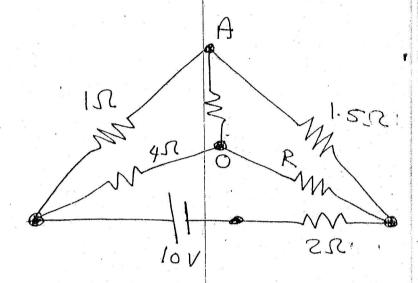


Tree 1

No of Loops = 5-2 = 3

Supernode

Super Loop

Super Loop

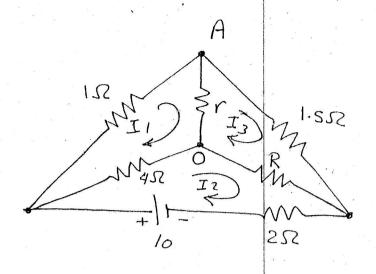

K.V.L for Loop 1

$$0 = I_1 + (I_1 - I_2) + (I_1 - I_3) r$$

$$0 = (5+r)I_1 - 4I_2 - rI_3$$

$$K v. l for loop 2$$


$$10 = (I_2 - I_1)^4 + I_2(i) + (I_2 - I_3)R$$

 $10 = -4I_1 + (6+R)I_2 - RI_3$
 $k.v.l. for loops$

$$0 = (I_3 - I_1)r + (I_3 - I_2)R + 1.5 I_3$$

$$0 = -rI_1 - RI_2 + (1.5 + R + r)I_3$$
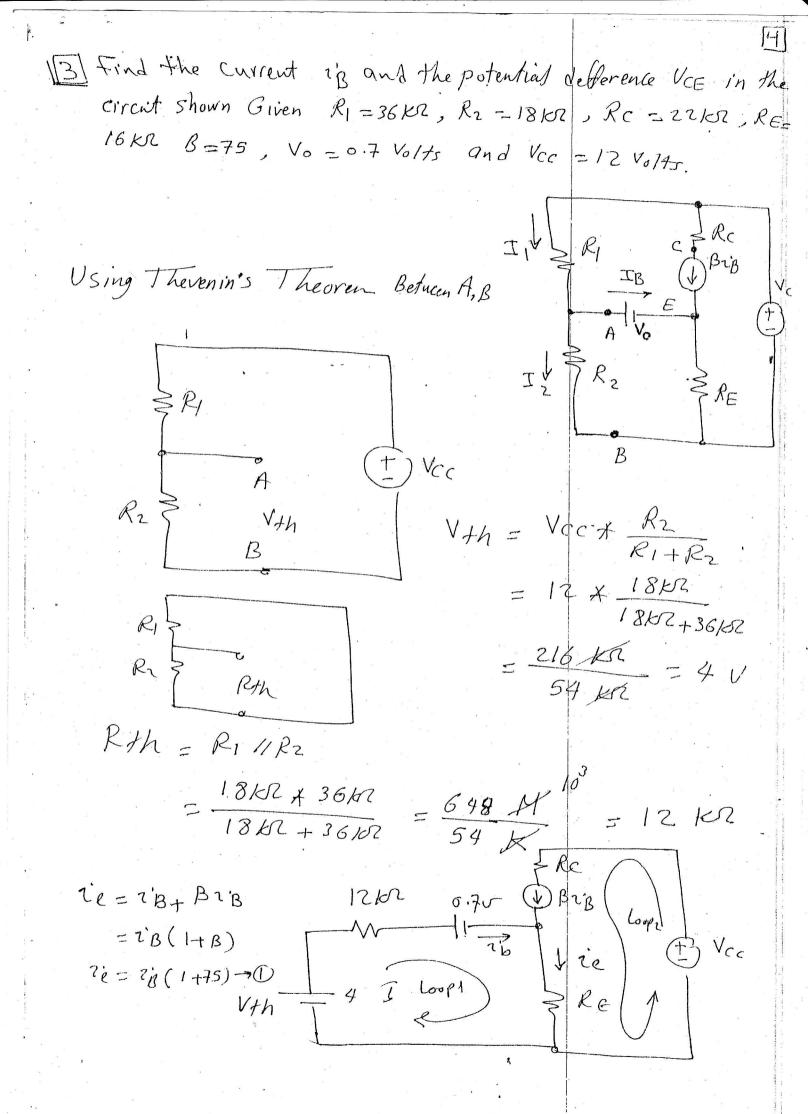
$$\begin{bmatrix} G \\ 1G \end{bmatrix} = \begin{bmatrix} 5+r & -4 & -r \\ -4 & 6+R & -R \\ -r & -R & 1.5+R+r \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \end{bmatrix}$$




$$V_{th} - 0.7 = \frac{2i3(12101) + 2i8(1+75)RE}{2i8 = \frac{12k + 76 \times 16 \times 12}{1228} = \frac{3.3}{1228} = 2.6 \text{ MA}.$$

K. U. L for Loop? $V_{CC} = BiB(RC) + VCE + ieRE$ $V_{CE} = V_{CC} - iB(BRC + (1+B)RE)$ $V_{CE} = V_{CC} - 2.6MA(75 \times 22 \times 10^{3} + 76 \times 16 \times 10^{3})$ $V_{CE} = 4-5V$


4

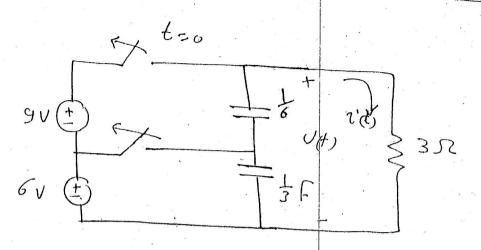if the switch is opened at t = o find the variables it) and Ut) what is the total energy stored in the circuit out t=0.



4 < 0

$$2(0) = \frac{15}{3}$$

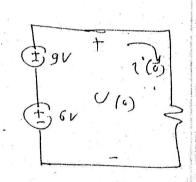

t>0

$$Ce_{9} = \frac{\frac{1}{6} * \frac{1}{3}}{\frac{1}{6} * \frac{1}{3}} = \frac{1}{9}$$

K. (- lat (4).

$$0 = \frac{c(t)}{3} + \frac{1}{9} \frac{dc(t)}{dt}$$

$$0 = 3 \text{ V(t)} + d \text{ V(t)} \longrightarrow \text{ V(t)} = \text{ Ke}$$

$$\sqrt{p(t)} = 0$$

$$\sigma(0) = 15 = k \rightarrow k = 15$$

$$7(t) = \frac{c(t)}{3} = \frac{15}{3}e^{-3t} = 5e^{-3t}$$

Draw the phasor diagram.

$$2 = R + X_L + X_C$$

$$= R + JWL = \frac{-J}{Wc}$$

$$I = \frac{V}{Z} = \frac{22010}{10/36.86} = 22/36.86$$

$$S = V.I^*$$

= 220 x 22 \(\frac{136.86}{36.86}\)
= 4846 \(\frac{136.86}{36.86}\)
 $S = 3872 + j 2903.3$


Reactive Ult. Amp = 2903.3

$$\sqrt{R} = I + R = 22 \frac{1-36.86}{86} \times 8$$

$$V_{L} = I \times X_{L} = 22 \frac{1}{-36.86} \times 20 \frac{190}{}$$

$$V_{C} = I \times X_{C} = 22 \frac{1}{-36.86} \times (4 \frac{1}{2})^{-90}$$

$$V_{C} = 308 \frac{1}{-126.86}$$

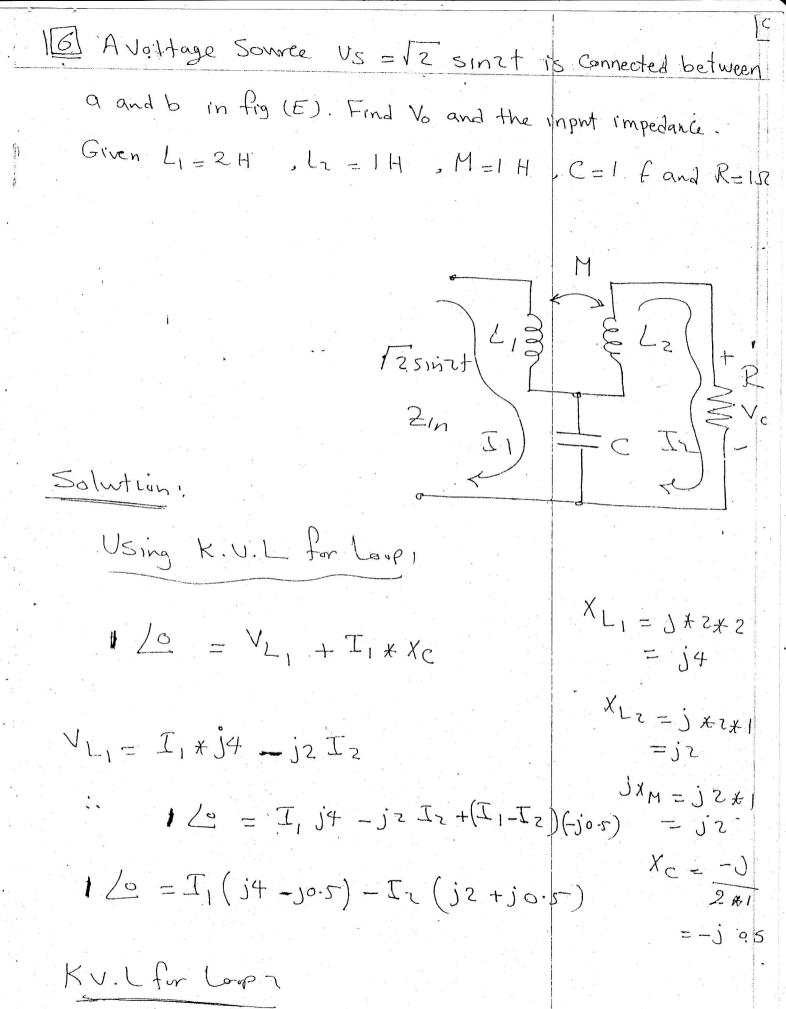

0 = (Iz II) (-jo.5) + Viz + Iz + I

$$0 = (I_{2} - I_{1})(-o.J) + I_{2}(J_{2}) - J_{2}I_{1} + I_{2}$$

$$0 = -1.5JI_{1} + (H1.5J)I_{2}$$

$$I_{1}, I_{2} = I_{2} + R$$


$$= I_{2} + R$$


$$= I_{2} + R$$

$$\begin{bmatrix} 120 \\ 0 \end{bmatrix} = \begin{bmatrix} j3.5 \\ -1.5j \end{bmatrix} \begin{bmatrix} 1\\ 1 \end{bmatrix}$$

1 + 1 · s j

elgjio

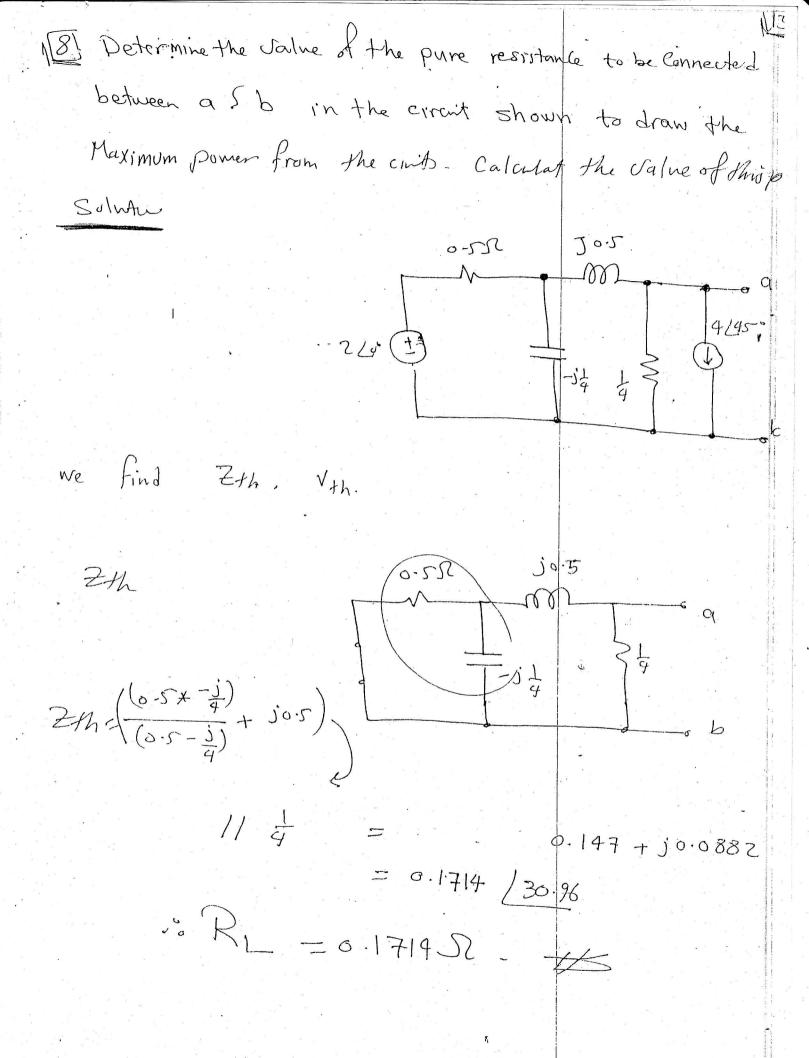

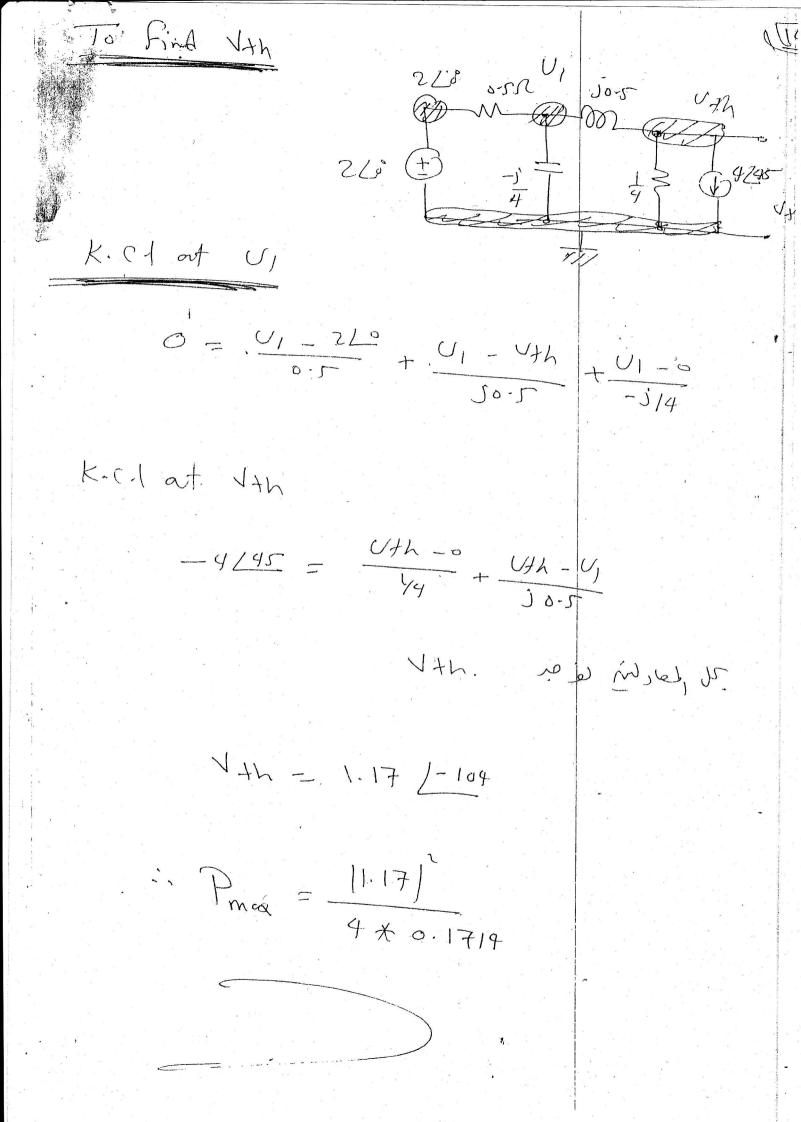

age ed 9 500 udlew